

An industrial sensor used to measure temperature, the Rosemount 214C from Emerson, has a nominal resistance of $100\ \Omega$ at 0°C , with a temperature coefficient of resistance (α) equal to $3.85 \times 10^{-3}/^\circ\text{C}$. It is used to measure temperatures ranging from -45°C to 455°C . An alarm is to be raised when the temperature rises above 400°C – a red LED, with a cut-in voltage of $1.8\ \text{V}$ is to light up to indicate this status. If the maximum current through the LED is to be $10\ \text{mA}$, while that through the RTD is limited to $100\ \mu\text{A}$, design an appropriate circuit for this purpose, so that the output voltage will not be greater than $5\ \text{V}$. You are provided with $+15\text{V}$ supplies and may assume that all components are ideal.

1. A current source is modelled such that the current through the RTD is limited to $100\ \mu\text{A}$.

We will use a variable resistor (RTD) whose resistance varies according to temperature, which can be calculated by using the formula

$$R = R_{ref}[1 + \alpha(T - T_{ref})] \quad (1)$$

where R_{ref} is given as $100\ \Omega$ at $T_{ref} = 0^\circ\ \text{C}$.

$$\alpha = 3.85 \times 10^{-3} / ^\circ\text{C}.$$

So from (1) at temperatures:

-45°C	$R = 82\ \Omega$
400°C	$R = 256\ \Omega$
455°C	$R = 272\ \Omega$

At 400°C we calculated $R = 256\ \Omega$. After measuring the voltage at the non inverting terminal of the op amp, it is found to be 4.45mV . So to provide this voltage as the reference to the inverting terminal, we use a voltage divider circuit, we assume R_4 to be $30\ \Omega$ and R_3 to be $99970\ \Omega$. This voltage divider is connected to the inverting terminal. So the diode will start to conduct when the temperature reaches 400°C . A LED diode is connected to a $1\text{k}\Omega$ resistor to limit the current to 10mA . The output is taken across $R_6 = 500\ \Omega$ so that the output voltage doesn't exceed 5V . We can from the fig 1. that the output is high after resistor increases more than $256\ \Omega$.

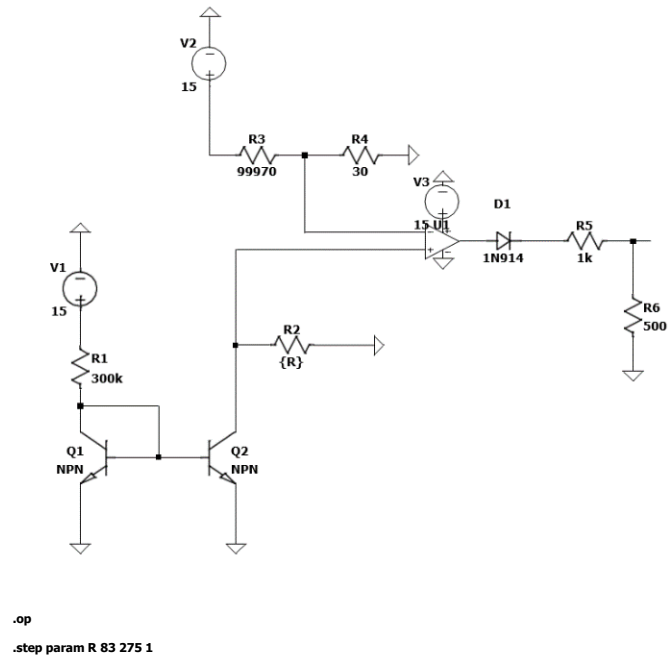


Fig 1.5

The fig 1.6 gives the relation between current through diode and the variable resistance.

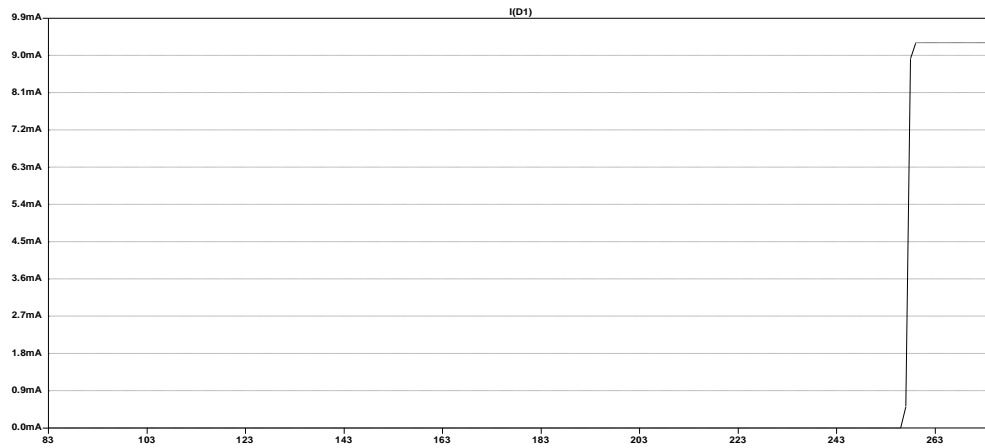


Fig 1.6

The fig 1.7 gives the relation between the output voltage and the variable resistance.

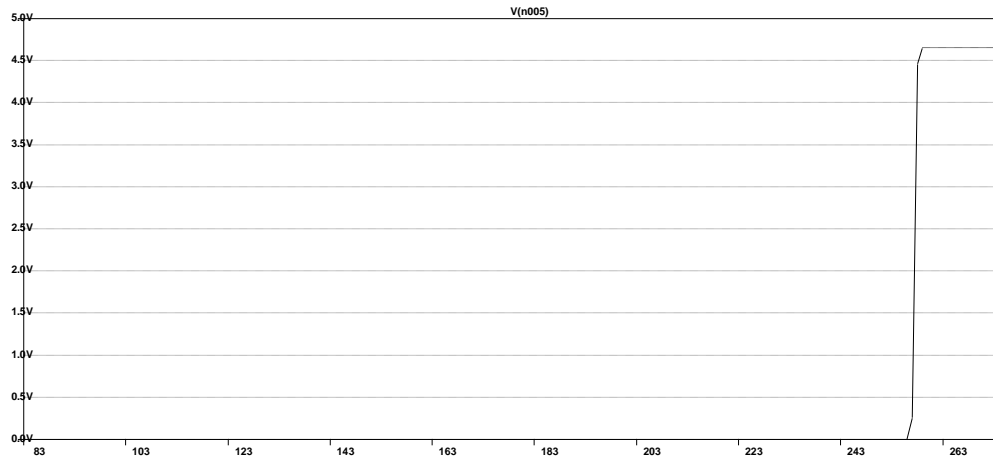


Fig 1.7

The safe range of operation of a temperature controlled chamber is to be indicated by means of a green LED which should glow when the temperature is between 25 and 45 degrees above the ambient temperature. A green LED has a typical forward cut-in voltage of 3.3 V. If the temperature sensor of choice is a Pt100 RTD, with a nominal value of resistance $R_0 = 100 \Omega$, temperature coefficient of resistance $\alpha = 3.85 \times 10^{-3} / ^\circ\text{C}$ and a maximum safe current of $100 \mu\text{A}$, design a circuit to obtain the above, provided that the maximum current through the LED is to be limited to 10 mA.

2. A current source is modelled such that the current through the RTD is limited to $100 \mu\text{A}$.

We will use a variable resistor (RTD) whose resistance varies according to temperature, which can be calculated by using the formula

$$R = R_{ref}[1 + \alpha(T - T_{ref})] \quad (1)$$

where R_{ref} is given as 100Ω at $T_{ref} = 0^\circ \text{C}$.

$$\alpha = 3.85 \times 10^{-3} / ^\circ\text{C}.$$

So from (1) at temperatures:

25°C	109.625Ω
45°C	117.325Ω

Since the circuit should work and light the LED diode when the temperature is between 25°C and 45°C , we will implement based on the logic of window comparator. Therefore at 109.625Ω and 117.325Ω , we need to find out the corresponding voltages using the simulation. The voltage is around 2.25mV at 109.625Ω and at 117.325Ω the voltage is around 2.4mV . Therefore the reference voltages are 2.25mV and 2.4mV . To provide this voltage, we use voltage divider circuits. We assume R_4 to be 160Ω and find R_3 to be 999840Ω , similarly R_5 to be 150Ω and R_6 to be 999850Ω . An LED diode with $1\text{k}\Omega$ resistance is connected to limit the current through the diode to 10mA . We can see that from fig 1.8 from 109.625Ω to 117.325Ω , output becomes high.

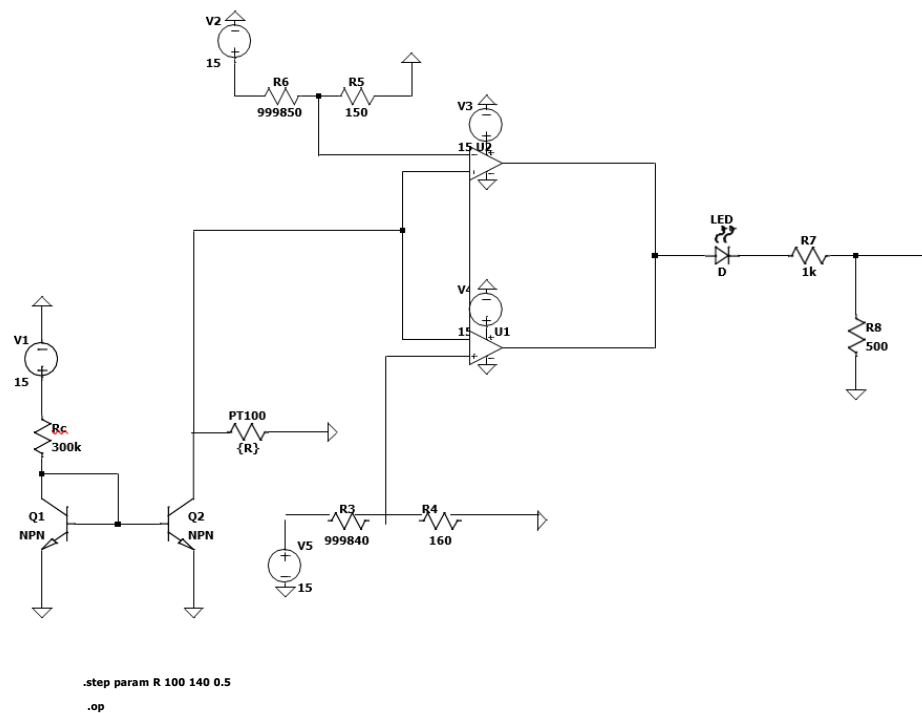


Fig 1.8

The fig 1.9 gives the relation between current through diode and the variable resistance.

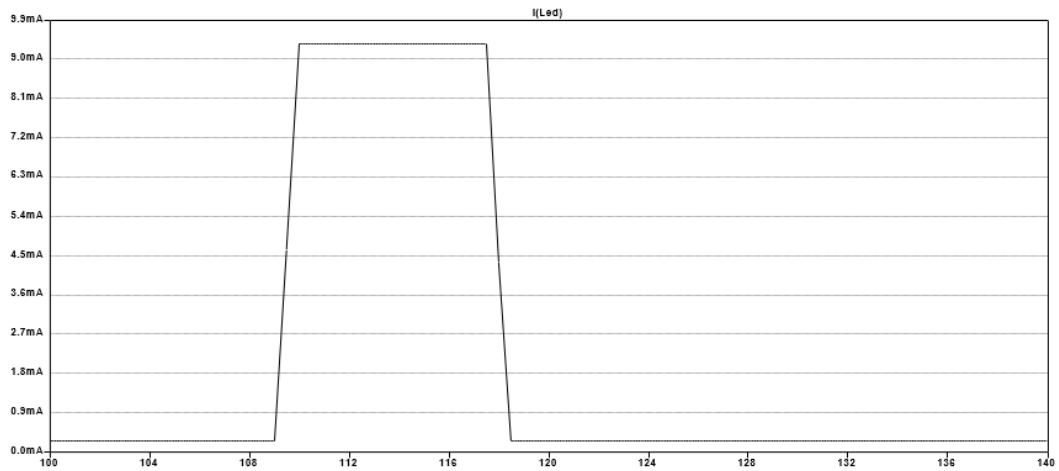


Fig 1.9

The fig 1.10 gives the relation between the output voltage and the variable resistance.

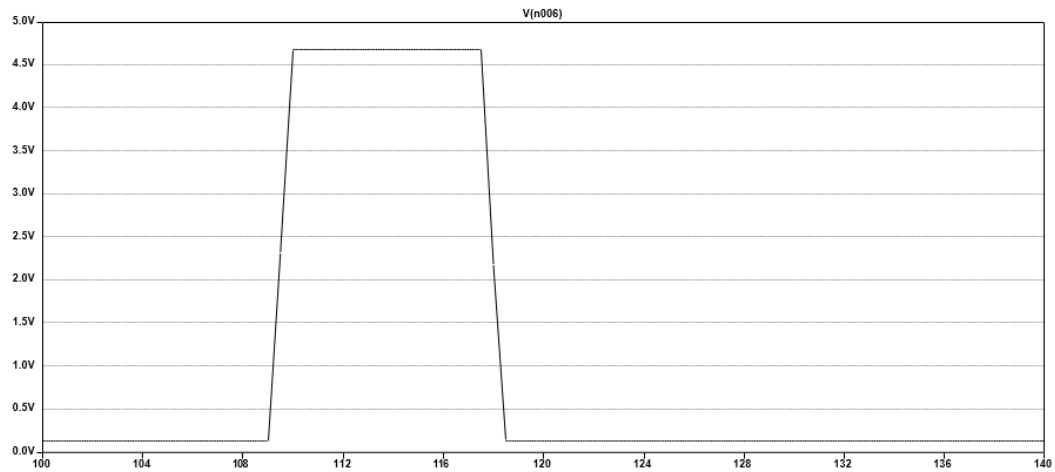


Fig 1.10